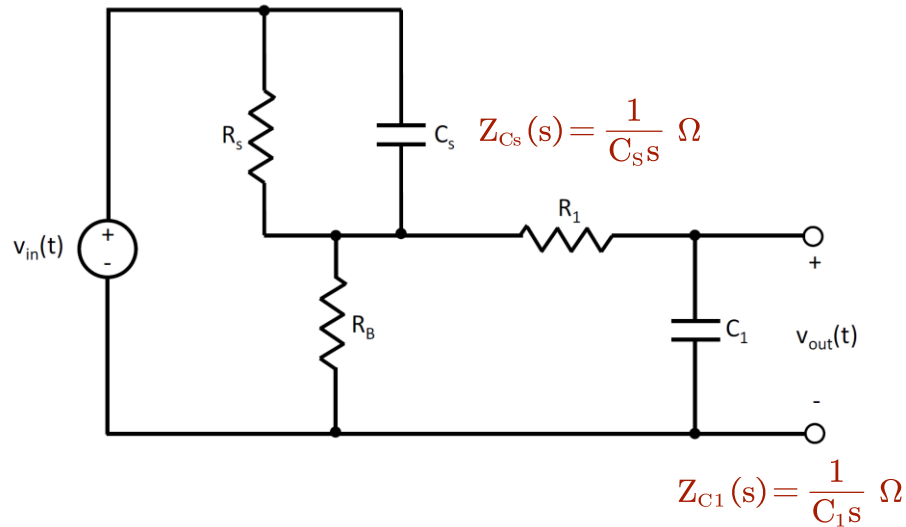


## ECE212 Homework 8

Tiange Zhai

November 24, 2021

Q1.



- a) Assume that the initial voltage of both capacitors is zero. Find  $v_{out}(s)/v_{in}(s)$ , expressing the numerator and denominator polynomials in expanded form with coefficients that are functions of the circuit elements in Fig. 1

As the circuit has zero initial conditions for all dynamic elements, its circuit diagram remains as it is with its elements expressed with their impedances in  $s$  domains (see above diagram). By inspections,  $R_s$  and  $C_s$  are connected in parallel (this circuit equivalent is denoted as  $Z_{eq1}$ ) while  $R_B$  and  $C_1$  with  $R_1$  are also connected in parallel (this circuit equivalent is denoted as  $Z_{eq2}$ ).  $Z_{eq1}$  and  $Z_{eq2}$  are then connected in series with the input voltage source. Therefore, the output voltage can be calculated using the principle of voltage division.

$$Z_{eq1} = Z_{R_s} || Z_{C_s} = \frac{Z_{R_s} \cdot Z_{C_s}}{Z_{R_s} + Z_{C_s}} = \frac{R_s \frac{1}{C_s s}}{R_s + \frac{1}{C_s s}}$$

$$Z_{eq2} = Z_{R_B} || (Z_{C_1} + Z_{R_1}) = R_B || \left( \frac{1}{C_1 s} + R_1 \right) = \frac{R_B \left( \frac{1}{C_1 s} + R_1 \right)}{\frac{1}{C_1 s} + R_1 + R_B}$$

$$\begin{aligned}
V_{out}(s) &= \frac{Z_{eq2}}{Z_{eq1} + Z_{eq2}} \cdot \frac{Z_{C1}}{Z_{R1} + Z_{C1}} \cdot V_{in}(s) \\
&= \frac{\frac{R_B \left( \frac{1}{C_1 s} + R_1 \right)}{\frac{1}{C_1 s} + R_1 + R_B}}{\frac{R_s \frac{1}{C_s s}}{R_s + \frac{1}{C_s s}} + \frac{R_B \left( \frac{1}{C_1 s} + R_1 \right)}{\frac{1}{C_1 s} + R_1 + R_B}} \cdot \frac{\frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} \cdot V_{in}(s) \\
&= \frac{\frac{R_B \left( \frac{1}{C_1 s} + R_1 \right)}{\frac{1}{C_1 s} + R_1 + R_B}}{\frac{R_s \frac{1}{C_s s} \left( \frac{1}{C_1 s} + R_1 + R_B \right) + R_B \left( \frac{1}{C_1 s} + R_1 \right) \left( R_s + \frac{1}{C_s s} \right)}{\left( R_s + \frac{1}{C_s s} \right) \left( \frac{1}{C_1 s} + R_1 + R_B \right)}} \cdot \frac{\frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} \cdot V_{in}(s) \\
&= \frac{R_B \left( R_s + \frac{1}{C_s s} \right) \frac{1}{C_1 s}}{R_s \frac{1}{C_s s} \left( \frac{1}{C_1 s} + R_1 + R_B \right) + R_B \left( \frac{1}{C_1 s} + R_1 \right) \left( R_s + \frac{1}{C_s s} \right)} \cdot V_{in}(s) \\
&= \frac{R_B \left( R_s s + \frac{1}{C_s} \right) \frac{1}{C_1}}{R_s \frac{1}{C_s} \left( \frac{1}{C_1} + R_1 s + R_B s \right) + R_B \left( \frac{1}{C_1} + R_1 s \right) \left( R_s s + \frac{1}{C_s} \right)} \cdot V_{in}(s)
\end{aligned}$$

Therefore,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_B \left( R_s s + \frac{1}{C_s} \right) \frac{1}{C_1}}{R_s \frac{1}{C_s} \left( \frac{1}{C_1} + R_1 s + R_B s \right) + R_B \left( \frac{1}{C_1} + R_1 s \right) \left( R_s s + \frac{1}{C_s} \right)}$$

**b) Substitute in  $R_s = 1.5 \text{ k}\Omega$ ,  $C_s = 220 \text{ nF}$ ,  $R_B = 500 \text{ }\Omega$ ,  $R_1 = 10 \text{ k}\Omega$  and  $C_1 = 22 \text{ nF}$ , and find the poles and zeros of  $v_{out}(s)/v_{in}(s)$**

Given the definition that zeros are roots of the numerator, the zeros of  $\frac{V_{out}(s)}{V_{in}(s)}$  can be calculated when the

numerator equals 0, e.g.,  $R_B \left( R_s s + \frac{1}{C_s} \right) \frac{1}{C_1} = 0$ :

$$\begin{aligned}
R_B \left( R_s s + \frac{1}{C_s} \right) \frac{1}{C_1} = 0 &\Rightarrow 500 \left( 1500 \cdot s + \frac{1}{220 \cdot 10^{-9}} \right) \frac{1}{22 \cdot 10^{-9}} = 0 \\
s &= -\frac{100000}{33} = -3030.3
\end{aligned}$$

Also, noticed that the denominator has a higher degree for variable  $s$  (degree of 2) while the numerator only has a degree of 1, this means that when  $s$  approaches infinity, the value of  $\frac{V_{out}(s)}{V_{in}(s)}$  will approach 0.

Given that  $\lim_{s \rightarrow \infty} \frac{V_{out}(s)}{V_{in}(s)} = 0$ , another zero can be found at  $s = \infty$ .

On the other hand, given the definition that poles are roots of the denominator, the poles of  $\frac{V_{out}(s)}{V_{in}(s)}$  can be

calculated when the denominator equals 0, e.g.,  $R_s \frac{1}{C_s} \left( \frac{1}{C_1} + R_1 s + R_B s \right) + R_B \left( \frac{1}{C_1} + R_1 s \right) \left( R_s s + \frac{1}{C_s} \right) = 0$ :

$$R_s \frac{1}{C_s} \left( \frac{1}{C_1} + R_1 s + R_B s \right) + R_B \left( \frac{1}{C_1} + R_1 s \right) \left( R_s s + \frac{1}{C_s} \right) = 0$$

$$1500 \frac{1}{220 \cdot 10^{-9}} \left( \frac{1}{22 \cdot 10^{-9}} + 10000s + 500s \right) + 500 \left( \frac{1}{22 \cdot 10^{-9}} + 10000s \right) \left( 1500s + \frac{1}{220 \cdot 10^{-9}} \right) = 0$$

$$7500000000s^2 + \frac{141250000000000s}{11} + \frac{500000000000000000}{121} = 0$$

$$s_1 = -12825, s_2 = -4295.9$$

Therefore, for the function  $\frac{V_{out}(s)}{V_{in}(s)}$ , two zeros can be found at  $s = -3030.3$  and  $s = \infty$ , and two poles can be found at  $s = -12825$ ,  $s = -4295.9$ .

**c) If  $v_{in}(t) = 10u(t)$ , find  $v_{out}(t)$ .**

By Laplace transform:

$$V_{in}(t) = 10u(t) \Rightarrow V_{in}(s) = 10\mathcal{L}\{u(t)\} = \frac{10}{s}$$

Using result from part a and part b:

$$V_{out}(s) = \frac{R_B \left( R_s s + \frac{1}{C_s} \right) \frac{1}{C_1}}{R_s \frac{1}{C_s} \left( \frac{1}{C_1} + R_1 s + R_B s \right) + R_B \left( \frac{1}{C_1} + R_1 s \right) \left( R_s s + \frac{1}{C_s} \right)} \cdot V_{in}(s)$$

$$= \frac{\frac{125000000000000}{121} (33s + 100000)}{7500000000 (s + 12825) (s + 4295.9)} \cdot \frac{10}{s}$$


$$= 1377.41 \frac{(33s + 100000)}{(s + 12825) (s + 4295.9)} \cdot \frac{1}{s}$$

$$\begin{aligned}
 &= 1377.41 \left( 0.00182 \cdot \frac{1}{s} - 0.00295 \cdot \frac{1}{s + 12825} + 0.00114 \cdot \frac{1}{s + 4295.9} \right) \\
 &= 2.50 \cdot \frac{1}{s} - 4.07 \cdot \frac{1}{s + 12825} + 1.57 \cdot \frac{1}{s + 4295.9}
 \end{aligned}$$


Using inverse Laplace transform to covert from s-domain to time domain:

$$\begin{aligned}
 V_{out}(t) &= \mathcal{L}^{-1}\{V_{out}(s)\} \\
 &= \mathcal{L}^{-1}\left\{2.50 \cdot \frac{1}{s} - 4.07 \cdot \frac{1}{s + 12825} + 1.57 \cdot \frac{1}{s + 4295.9}\right\} \\
 &= 2.50 \mathcal{L}^{-1}\left\{\frac{1}{s}\right\} - 4.07 \mathcal{L}^{-1}\left\{\frac{1}{s + 12825}\right\} + 1.57 \mathcal{L}^{-1}\left\{\frac{1}{s + 4295.9}\right\} \\
 &= 2.50 \cdot u(t) - 4.07 \cdot e^{-12825t} \cdot u(t) + 1.57 \cdot e^{-4295.9t} \cdot u(t) \\
 &= (2.50 - 4.07 \cdot e^{-12825t} + 1.57 \cdot e^{-4295.9t}) u(t)
 \end{aligned}$$

Q2.

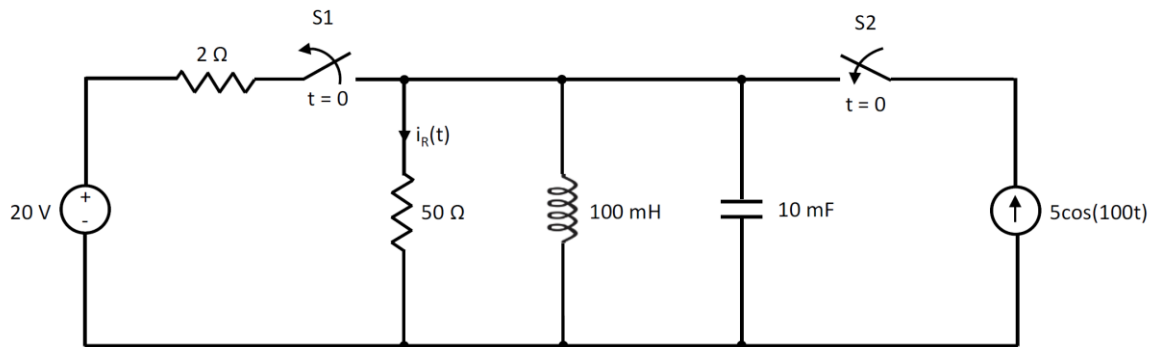

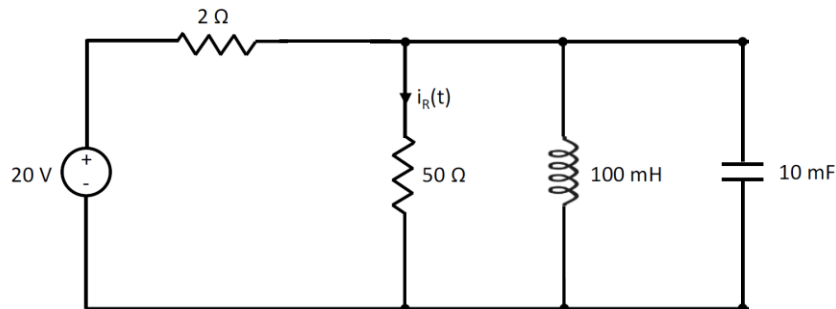- a) Draw the circuit for  $t < 0$  and find the initial conditions of inductor current and capacitor voltage.




At steady state, capacitor can be seen as an open circuit, and inductor can be seen as a short circuit. As a result, in the redrawn circuit, the  $50\Omega$  resistor is shorted by the inductor at steady state. Therefore:

$$V_C(0^-) = 0V$$

$$I_L(0^-) = \frac{20}{2} = 10A$$

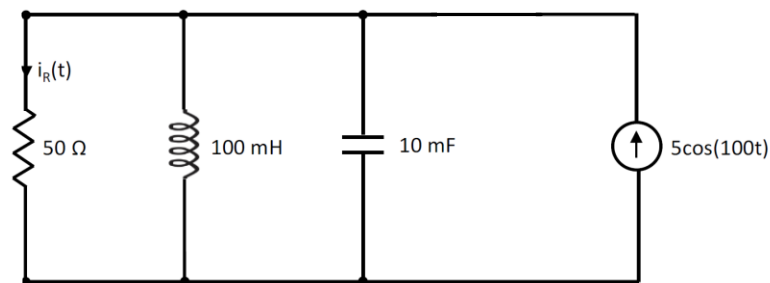**b) Draw the circuit for  $t > 0$  in the s-domain.**

Redrawn the schematic as below (in time domain):



Converting time domain circuit elements to s-domain:

Current source:

$$I_{sc}(s) = \mathcal{L}\{I_{sc}(t)\} = 5\mathcal{L}\{\cos(100t)\} = \frac{5s}{s^2 + 10000} A$$


Inductor impedance:

$$Z_L(s) = Ls = 0.1s = \frac{s}{10} \Omega$$

Capacitor impedance:

$$Z_C(s) = \frac{1}{Cs} = \frac{1}{0.01s} = \frac{100}{s} \Omega$$

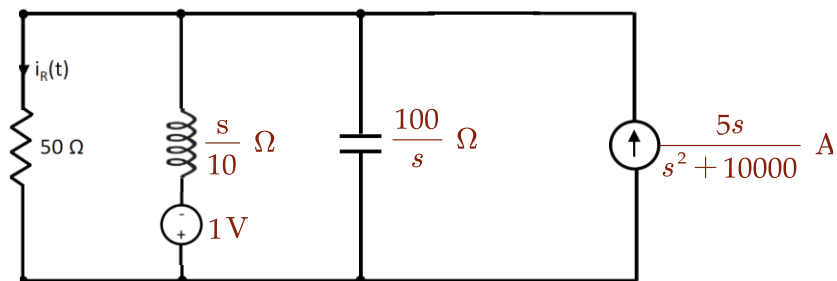
Also, as seen in part a, the initial condition for inductor is non-zero. Therefore, in s-domain, a new voltage source that has value of  $V_{L0} = Li_L(0^-) = \frac{1}{10} \cdot 10 = 1V$  must be added in the schematics in s-domain as follows:



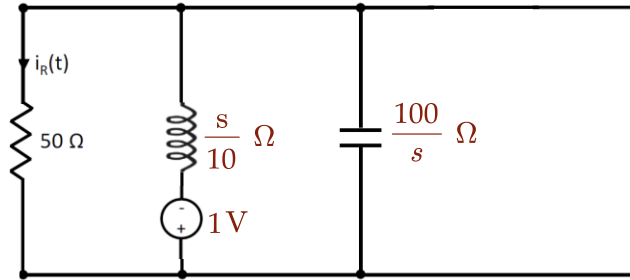c) Find the value of  $i_R(t)$  for  $t > 0$ .

Using superposition to calculate both the zero-input response and the zero-state response:

Zero-Input response (where all original sources are turned off):



By KVL:  $V_{R||C} + V_L = -1$

$$Z_{eq} = \frac{50 \cdot \frac{100}{s}}{50 + \frac{100}{s}} = \frac{\frac{5000}{s}}{\frac{50s + 100}{s}} = \frac{100}{s + 2} \Omega$$

$$I_R(s) = \frac{V_R(s)}{R}$$

$$= -1 \cdot \frac{\frac{100}{s+2}}{\frac{100}{s+2} + \frac{s}{10}} \cdot \frac{1}{50}$$

$$= -\frac{1}{50} \cdot \frac{1000}{1000 + s^2 + 2s}$$

$$= -\frac{20}{s^2 + 2s + 1000} = -\frac{20}{3\sqrt{111}} \cdot \frac{3\sqrt{111}}{(s+1)^2 + 999}$$


$$i_R(t) = \mathcal{L}^{-1}\{I_R(s)\}$$

$$= \mathcal{L}^{-1}\left\{-\frac{20}{3\sqrt{111}} \cdot \frac{3\sqrt{111}}{(s+1)^2 + 999}\right\}$$

$$= -\frac{20}{3\sqrt{111}} \cdot \mathcal{L}^{-1}\left\{\frac{3\sqrt{111}}{(s+1)^2 + 999}\right\}$$

$$= -0.633e^{-t} \sin(31.607t) \text{ A} = -0.633e^{-t} \cos(-31.607t + 90^\circ) \text{ A}$$

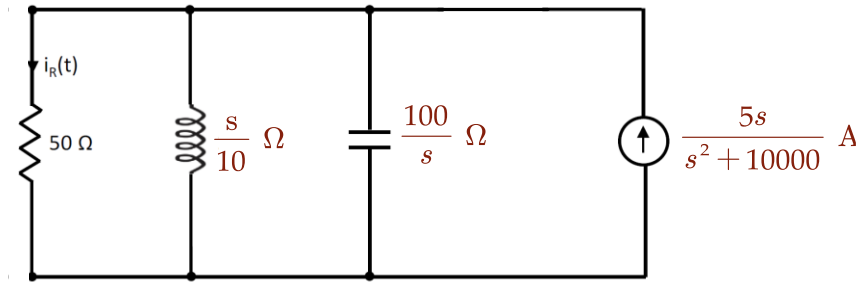Zero-State response (where all sources resulting from initial conditions are turned off):



Using current division principle:

$$Z_{L||C} = \frac{\frac{s}{10} \cdot \frac{100}{s}}{\frac{s}{10} + \frac{100}{s}} = \frac{10}{\frac{s^2 + 1000}{10s}} = \frac{100s}{s^2 + 1000}$$

$$I_R(s) = \frac{Z_{L||C}}{Z_{L||C} + Z_R} \cdot I_{SC}(s) = \frac{\frac{100s}{s^2 + 1000}}{\frac{100s}{s^2 + 1000} + 50} \cdot I_{SC}(s) = \frac{2s}{(s+1)^2 + 999} \cdot I_{SC}(s)$$

Calculating the sinusoidal steady-state response:

$$T(s) = \frac{I_R(s)}{I_{SC}(s)} = \frac{2s}{(s+1)^2 + 999}$$

$$\Rightarrow T(j\omega) = T(j100) = \frac{j200}{(j100+1)^2 + 999} = 0.0222 \angle -88.73^\circ$$

$$\Rightarrow i_R(t) = 5 \cdot 0.0222 \cos(100t + 0^\circ - 88.73^\circ) A = 0.111 \cos(100t - 88.73^\circ) A$$

Therefore, by superposition principle, the total response is:

$$i_R(t) = -0.633e^{-t} \cos(-31.607t + 90^\circ) + 0.111 \cos(100t - 88.73^\circ) A$$

- d) Use phasor analysis to verify the magnitude and phase of the steady-state component of  $i_R(t)$  which you found in part c.**

Converting circuit into phasor domains:


Current source:

$$I_{sc} = 5 \angle 0^\circ$$

Impedances:

$$Z_L = j\omega L = j \cdot 100 \cdot 0.1 = j10 \Omega$$
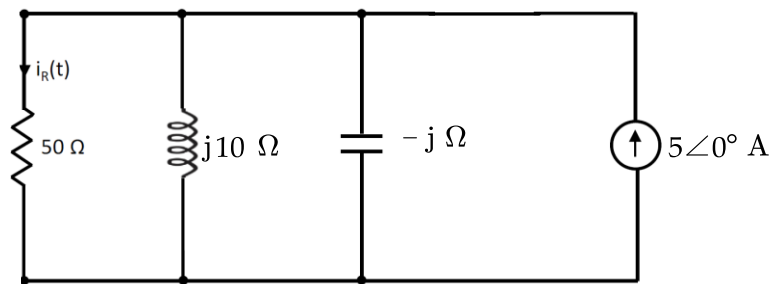
$$Z_C = -j \frac{1}{\omega C} = -j \cdot \frac{1}{100 \cdot 0.01} = -j \Omega$$



Calculating  $I_R(t)$ :

$$Z_{RLC} = Z_R || Z_L || Z_C \Rightarrow \frac{1}{Z_{RLC}} = \frac{1}{50} + \frac{1}{j10} + \frac{1}{-j} \Rightarrow Z_{RLC} = 1.11 \angle -88.73^\circ \Omega$$

$$V_R = I_{SC} \cdot Z_{RLC} = 5 \angle 0^\circ \cdot 1.11 \angle -88.73^\circ = 5.55 \angle -88.73^\circ \text{ V}$$

$$I_R = \frac{V_R}{Z_R} = \frac{5.55 \angle -88.73^\circ}{50} = 0.111 \angle -88.73^\circ \text{ A}$$

Converting from phasor domain to time domain:

$$I_R = 0.111 \angle -88.73^\circ \text{ A} \Rightarrow i_R(t) = 0.111 \cos(100t - 88.73^\circ) \text{ A}$$

The magnitude and phase of the steady-state component of  $i_R(t)$  calculated in phasor domain aligns with the s-domain analysis from part c.