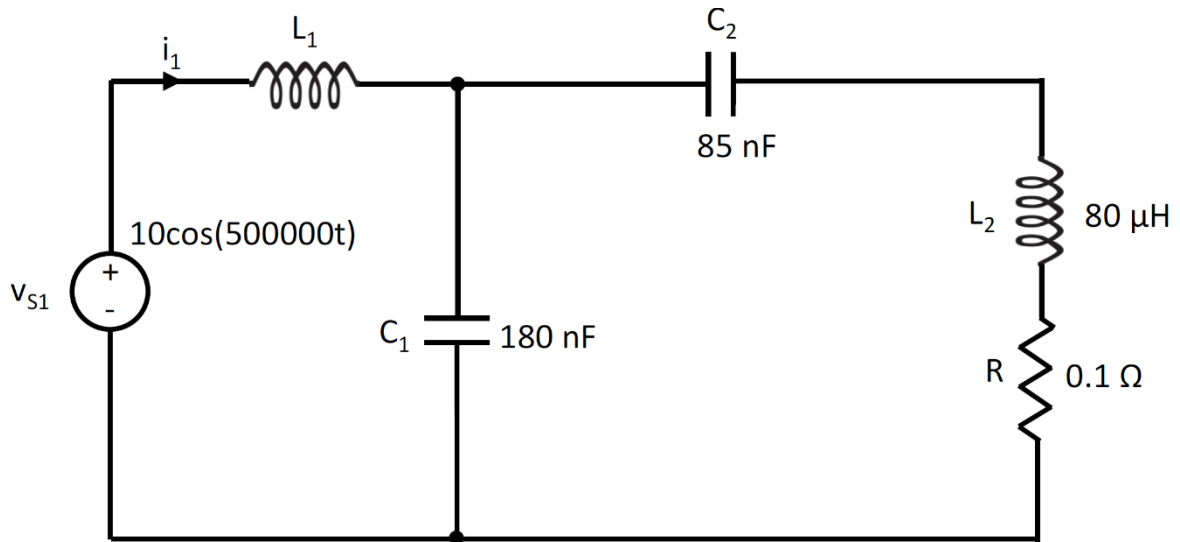


ECE212 Homework 5

Tiange Zhai

Oct 16, 2021

Q1.



1. Calculate the equivalent impedance Z_{eq1} formed by the combination of C_2 , L_2 and R .

$$Z_{C2} = \frac{1}{j\omega C} = \frac{1}{j \cdot 5 \times 10^5 \cdot 85 \times 10^{-9}} = -j \frac{1}{425} \times 10^4 \Omega = -j23.529 \Omega$$

$$Z_{L2} = j\omega L = j \cdot 5 \times 10^5 \cdot 80 \times 10^{-6} = j40 \Omega$$

$$Z_R = R = 0.1 \Omega$$

As C_2 , L_2 and R are connected in series according to above circuit configuration, the equivalent impedance Z_{eq1} can be calculated by simple addition as follows:

$$Z_{eq1} = Z_{C2} + Z_{L2} + Z_R = -j23.529 \Omega + j40 \Omega + 0.1 \Omega = 0.1 + j16.471 \Omega = 16.471 \angle 89.652^\circ \Omega$$

2. Calculate the equivalent impedance Z_{eq2} formed by the combination of Z_{eq1} and C_1 .

$$Z_{C1} = \frac{1}{j\omega C} = \frac{1}{j \cdot 5 \times 10^5 \cdot 180 \times 10^{-9}} = -j \frac{1}{9} \times 10^2 \Omega = -j11.11 \Omega$$

As Z_{eq1} and C_1 are connected in parallel, Z_{eq2} can be calculated as follows:

$$\begin{aligned} \frac{1}{Z_{eq2}} &= \frac{1}{Z_{eq1}} + \frac{1}{Z_{C1}} = \frac{1}{16.471 \angle 89.652^\circ} + \frac{1}{11.11 \angle -90^\circ} = \frac{1}{16.471} \angle -89.652^\circ + \frac{1}{11.11} \angle 90^\circ \\ &= 0.000368752 - j0.029309 = 0.0293113 \angle -78.759^\circ \end{aligned}$$

$$Z_{eq2} = \frac{1}{0.029 \angle -89.28} \Omega = 34.12 \angle -89.28^\circ \Omega = 0.429 - j34.13 \Omega$$

- 3. Design a value of L_1 which gives rise to a reactance with the same magnitude as the complex part of Z_{eq2} but with the opposite sign.**


From Part 2 it can be found that $Z_{eq2} = 0.429 - j34.13 \Omega$, which means $X_{eq2} = -j34.13 \Omega$.

$$\begin{aligned} X_{L1} &= -X_{eq2} = j34.13 \Omega \\ \Rightarrow j\omega L &= \text{Im}\{R_{L1}\} = X_{L1} \\ \Rightarrow L_1 &= \frac{X_{L1}}{j\omega} = \frac{j34.13}{j500000} = 68.26 \mu H \end{aligned}$$

- 4. Derive an expression for the supply current $i_1(t)$ (in the time domain, at sinusoidal steady state) if the value of L_1 calculated in part 3 is used.**

$$i_1(t) = \frac{V_{s1}(t)}{R_{eq2} + R_{L1}} = \frac{10 \cos(500000t)}{0.429} = 23.31 \cos(500000t) A$$

Q2.

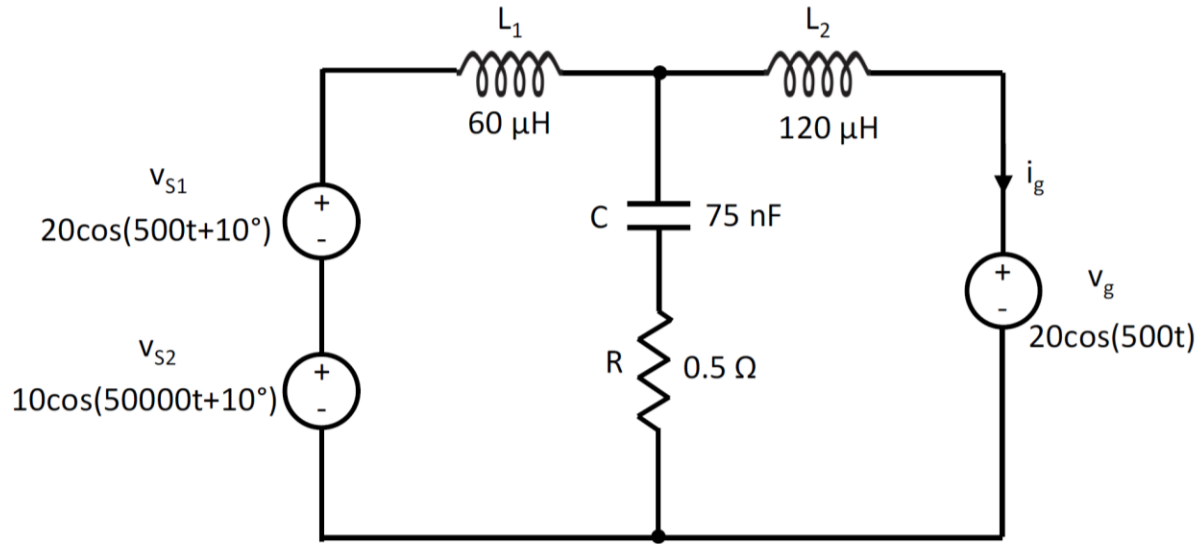

1. Calculate the impedance of all the dynamic elements in the circuit at $\omega_1 = 500 \text{ rad/s}$.


$$Z_{L_1} = j\omega L_1 = j \cdot 5 \times 10^2 \cdot 60 \times 10^{-6} = j0.03 \Omega = 0.03 \angle 90^\circ \Omega$$

$$Z_{L_2} = j\omega L_2 = j \cdot 5 \times 10^2 \cdot 120 \times 10^{-6} = j0.06 \Omega = 0.06 \angle 90^\circ \Omega$$

$$Z_{C_2} = \frac{1}{j\omega C} = \frac{1}{j \cdot 5 \times 10^2 \cdot 75 \times 10^{-9}} = -j \frac{1}{375} \times 10^7 \Omega = -j26.6667 k\Omega$$

$$Z_R = R = 0.5 \Omega$$

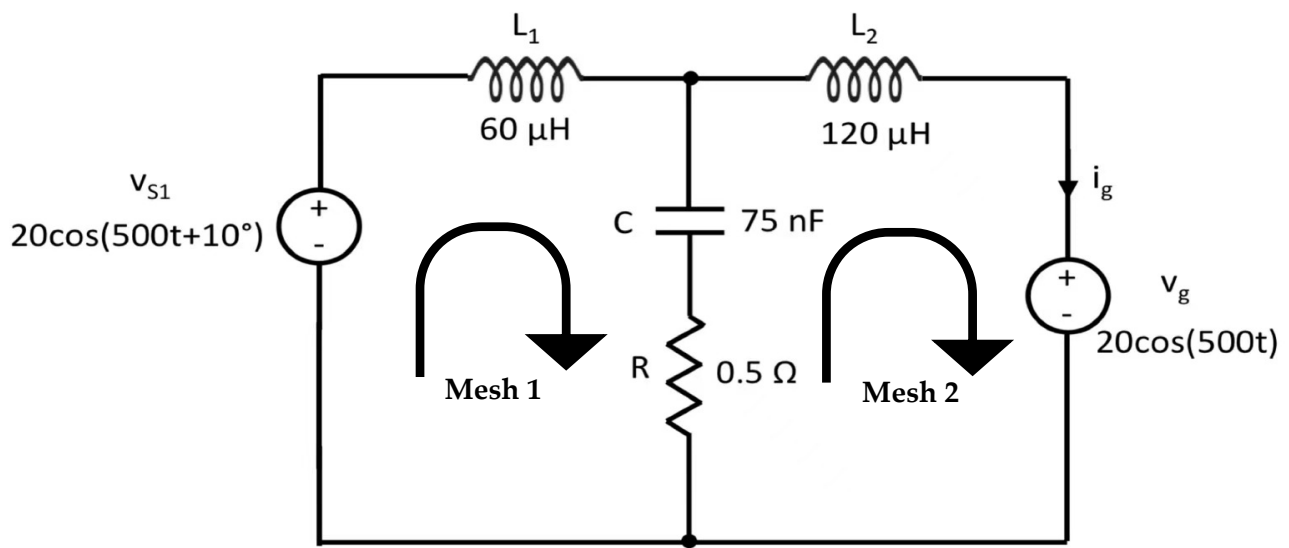2. Draw the phasor domain circuit diagram at ω_1 .



3. Calculate the phasor current $I_g^{(1)}$ at ω_1 .

First, transform the existing two voltage source into their phasor forms.

$$V_{s1} = 20 \cos(500t + 10^\circ) \Rightarrow \mathbf{V}_{s1} = 20 \angle 10^\circ V$$

$$V_g = 20 \cos(500t) \Rightarrow \mathbf{V}_g = 20 \angle 0^\circ V$$

Then, combine C and R to reduce complexity of the above configuration.

$$Z_{eq} = Z_R + Z_{C2} = 0.5 - j26666.7 \Omega = 26666.7 \angle -89.999^\circ$$

Using mesh analysis, at Mesh 1 (Mesh 1 has a mesh current of I_1), the following relationship can be found using KVL.

$$V_{L1} + V_C + V_R = V_{s1} \Rightarrow Z_{L1} \cdot I_1 + Z_{eq} \cdot (I_1 - I_2) = V_{s1}$$

$$0.03 \angle 90^\circ \cdot I_1 + 26666.7 \angle -89.999^\circ \cdot (I_1 - I_2) = 20 \angle 10^\circ \quad (1)$$

Using mesh analysis, at Mesh 2 (Mesh 2 has a mesh current of I_2), the following relationship can be found using KVL.

$$V_{L2} + V_C + V_R = -V_g \Rightarrow Z_{L2} \cdot I_2 + Z_{eq} \cdot (I_2 - I_1) = -V_g$$

$$0.06 \angle 90^\circ \cdot I_2 + 26666.7 \angle -89.999^\circ \cdot (I_2 - I_1) = -20 \angle 0^\circ \quad (2)$$

Solve the system of equation of (1)(2) by combining the two equations as follows.

$$0.03 \angle 90^\circ \cdot I_1 + 0.06 \angle 90^\circ \cdot I_2 = 20 \angle 10^\circ - 20 \angle 0^\circ$$

$$0.03 \angle 90^\circ \cdot I_1 + 0.06 \angle 90^\circ \cdot I_2 = -0.303845 + j3.47296 = 3.48623 \angle 95.00^\circ$$

$$\Rightarrow I_1 + 2I_2 = 116.208 \angle 5.00^\circ$$

$$\Rightarrow I_1 = 116.208 \angle 5.00^\circ - 2I_2 \quad (3)$$

Substituting (3) into (2),

$$0.06 \angle 90^\circ \cdot I_2 + 26666.7 \angle -89.999^\circ \cdot (3 \cdot I_2 - 116.208 \angle 5.00^\circ) = -20$$

$$I_2 = 38.736 \angle 5.00^\circ A \Rightarrow I_1 = 38.736 \angle 5.00^\circ A$$

$$i_g^{(1)} = I_2 = 38.736 \angle 5.00^\circ A = 38.736 \cos(500t + 5.00^\circ) A$$

4. Calculate the impedance of all the dynamic elements in the circuit at $\omega_2 = 50000 \text{ rad/s}$.


$$Z_{L1} = j\omega L_1 = j \cdot 5 \times 10^4 \cdot 60 \times 10^{-6} = j3\Omega = 3\angle 90^\circ \Omega$$

$$Z_{L2} = j\omega L_2 = j \cdot 5 \times 10^4 \cdot 120 \times 10^{-6} = j6\Omega = 6\angle 90^\circ \Omega$$

$$Z_{C2} = \frac{1}{j\omega C} = \frac{1}{j \cdot 5 \times 10^4 \cdot 75 \times 10^{-9}} = -j \frac{1}{375} \times 10^5 \Omega = -j266.667\Omega$$

$$Z_R = R = 0.5\Omega$$

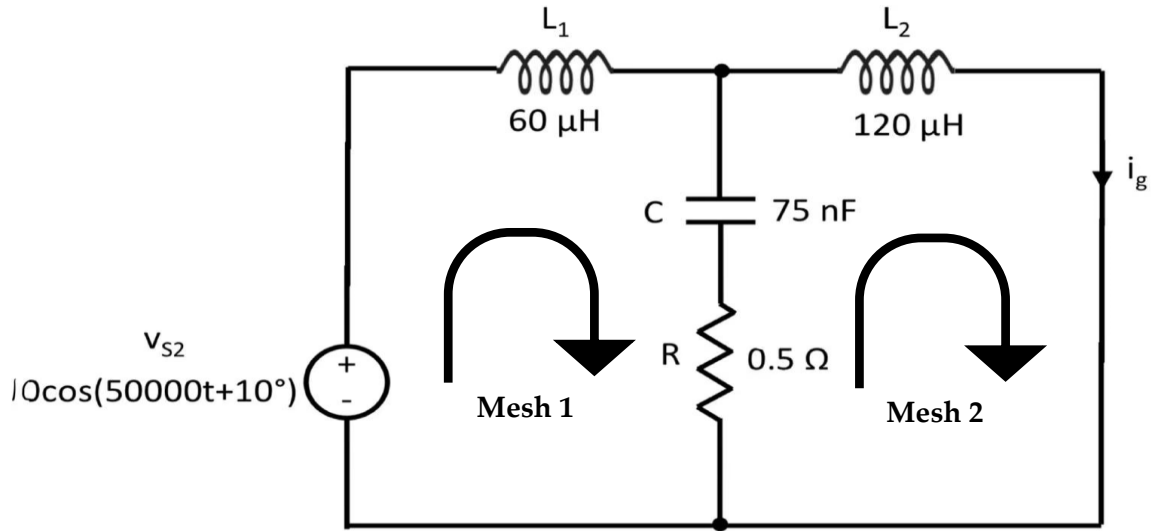5. Draw the phasor domain circuit diagram at ω_2 .



6. Calculate the phasor current $I_g^{(1)}$ at ω_1 .

First, transform the existing two voltage source into their phasor forms.

$$V_{s1} = 10\cos(50000t + 10^\circ) \Rightarrow \mathbf{V}_{s1} = 10\angle 10^\circ V$$

Then, combine C and R to reduce complexity of the above configuration.

$$Z_{eq} = Z_R + Z_{C2} = 0.5 - j266.667\Omega = 266.667\angle -89.893^\circ \Omega$$

Using mesh analysis, at Mesh 1 (Mesh 1 has a mesh current of I_1), the following relationship can be found using KVL.

$$V_{L1} + V_C + V_R = V_{s2} \Rightarrow Z_{L1} \cdot I_1 + Z_{eq} \cdot (I_1 - I_2) = V_{s2}$$

$$3\angle 90^\circ \cdot I_1 + 266.667\angle -89.893^\circ \cdot (I_1 - I_2) = 10\angle 10^\circ \quad (4)$$

Using mesh analysis, at Mesh 2 (Mesh 2 has a mesh current of I_2), the following relationship can be found using KVL.

$$\begin{aligned} V_{L2} + V_C + V_R &= 0 \Rightarrow Z_{L2} \cdot I_2 + Z_{eq} \cdot (I_2 - I_1) = 0 \\ 6 \angle 90^\circ \cdot I_2 + 266.667 \angle -89.893^\circ \cdot (I_2 - I_1) &= 0 \end{aligned} \quad (5)$$

Solve the system of equation of (4)(5) by combining the two equations as follows.

$$\begin{aligned} 3 \angle 90^\circ \cdot I_1 + 6 \angle 90^\circ \cdot I_2 &= 10 \angle 10^\circ \\ \Rightarrow I_1 + 2I_2 &= 3.33 \angle -80^\circ \\ \Rightarrow I_1 &= 3.33 \angle -80^\circ - 2I_2 \end{aligned} \quad (6)$$

Substituting (3) into (2),

$$\begin{aligned} 6 \angle 90^\circ \cdot I_2 + 266.667 \angle -89.893^\circ \cdot (3 \cdot I_2 - 3.33 \angle -80^\circ) &= 0 \\ I_2 &= 1.12 \angle -80.00^\circ A \Rightarrow I_1 = 1.09 \angle -80.00^\circ A \\ i_g^{(2)} = I_2 &= 1.12 \angle -80.00^\circ A = 1.12 \cos(50000t - 80.00^\circ) A \end{aligned}$$

7. Using the solutions for parts 3 and 6, calculate the time domain current $i_g(t)$ at sinusoidal steady state.

By the principle of superposition, the time domain current $i_g(t)$ can be calculated as the sum of the solution from parts 3 and 6 as follows:

$$i_g(t) = i_g^{(1)}(t) + i_g^{(2)}(t) = 38.736 \cos(500t + 5.00^\circ) + 1.12 \cos(50000t - 80.00^\circ) A$$